



Normal	READING**
EA	
REQ	
IT	
EREQ	
IR1	
IR2	
IR3	

R1 Open	READING**
EA	
REQ	
IT	
EREQ	
IR1	
IR2	
IR3	

R1 Short	READING**
EA	
REQ	
IT	
EREQ	
IR1	
IR2	
IR3	

- 1) R3 is open $R_T = \underline{\hspace{2cm}}$ and $I_T = \underline{\hspace{2cm}}$
- 2) R2 is short $E_{R1} = \underline{\hspace{2cm}}$ and $I_T = \underline{\hspace{2cm}}$
- 3) Any opening a circuit makes resistance $\underline{\hspace{2cm}}$ and current go $\underline{\hspace{2cm}}$
- 4) $R_{EQ} = 6K\Omega$ what is the malfunction?
- 5) $I_T = 7 \text{ mA}$ what is the malfunction?
 $R_{EQ} = \underline{\hspace{2cm}}$ $E_A = \underline{\hspace{2cm}}$ $I_T = \underline{\hspace{2cm}}$